

Tyler Crowley

CS300

Tireman

22 April, 2022

### Final Project Writeup

The purpose of this project was to create a self-regulating fan to cool a thermistor variable-resistor being heated by a second resistor placed just below it. An Arduino takes in an input reading from the thermistor and, using a set of assembly instructions that compares the input to a preset reference voltage representing the desired temperature for the thermistor, adjusts the fan's speed accordingly. It then sends the new signal frequency to a circuit which turns the Arduinos 5V output into a matching 12V signal to run the fan, whilst simultaneously outputting the voltage through a pair of BCD Encoders to a set of 7 segments displays, as an ASCII code. In the code, the user can set the minimum and maximum speed of the fan using `minDutyCycle` and `maxDutyCycle`, as well as change the temperature of the thermistor through the variable input running through the resistor underneath it.

#### Fan Circuit:

The wire from Digital Pin 4 runs through a  $100\Omega$  resistor, then splits into 2 transistors, the top one runs up to the fan and joins with the 12V power supply, the bottom one leads to ground. Both meet in the middle run through a  $10\Omega$  resistor into a MOSFET, which runs one end to ground, and the other into the ground wire of the fan. Between the 2 fan wires is the schottky diode, which runs from the ground to positive wires, and serves as a discharge spot for any leftover power when the circuit is turned off. The thermistor runs from power into a  $10k\Omega$

resistor, between the two is also the wire which runs to Analog Pin 0 on the Arduino, the resistor then runs to ground. The  $150\Omega$  resistor acts as your heat source, this runs from a variable input set at  $\approx 20V$ , to ground. The thermistor should be on top of and touching this resistor for it to heat up properly.

#### Voltage Output:

Port C on the Arduino (pins 30-37) should run through a pair of BCD Decoders. Pin 30 should connect to input D of your left or highest significance display's decoder, and pin 37 should run into input A on your least significant one. The rest fall between the two in their logical order. The output should all be run through a generic resistor pack, so as to not blow out the LEDs, then into their respective input on the 7 segment displays.

#### Parts List:

- 1 x Arduino Mega 2560
- 1 x 12V Fan
- 1 x Thermistor
- 2 x BCD Decoders
- 2 x Resistor Packs
- 2 x 7-Segment Displays
- 1 x MOSFET
- 2 x Transistors
- 1 x Schottky Diode
- 1 x  $10,000\Omega$  Resistor
- 1 x  $150\Omega$  Resistor
- 1 x  $100\Omega$  Resistor
- 1 x  $10\Omega$  Resistor
- 1 x 5V DC Power Source
- 1 x 12V DC Power Source
- 1 x Variable DC Power Source
- A lot of wires